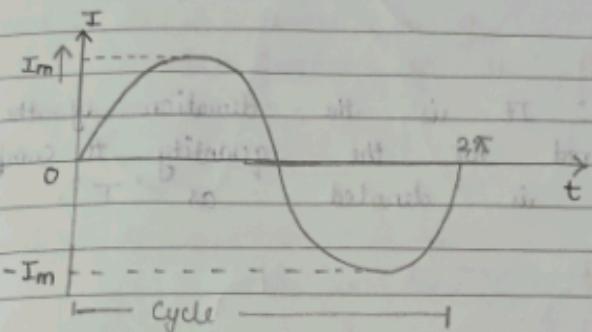


Date.....

Unit - 2 : AC circuit


Alternate current (AC) :-

The AC means alternate current. A current reversed its direction periodically. The mathematically representation as — $I = I_0 \sin \omega t$ or $I = I_m \sin \omega t$



Terminology :

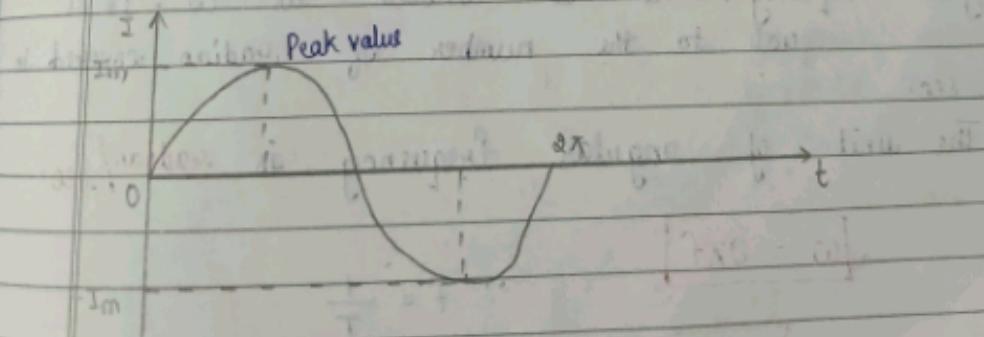
1. Cycle : The value of sin wave repeat after every 2π radians. One complete set of positive and negative values of the function is c/o a cycle.
2. Peak value : Peak value is the maximum value denoted as I_m , +ve and -ve of the quantity.




Spiral

Date.....

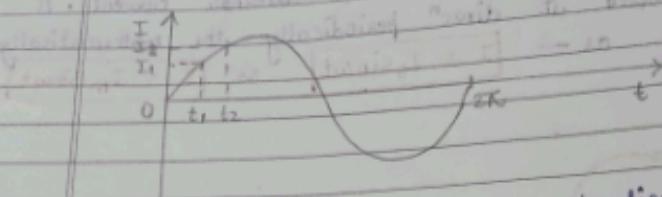3. Instantaneous value : It is the value of quantity at any instant w.r.t. to time. It is known as instantaneous value.



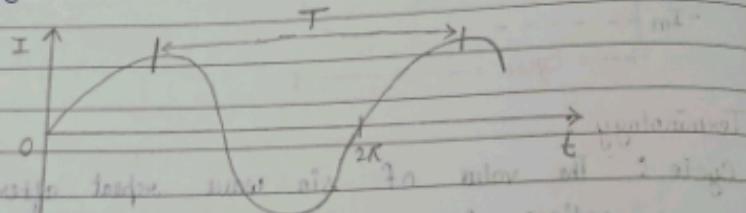4. Time period : It is the duration of the time required for the quantity to complete one cycle. It is denoted as 'T'.



5. Frequency : Frequency is the number of cycles occurring in one second.

$$f = \frac{1}{T} \quad \text{Hz}$$

6. Angular frequency : It is denoted as ' ω '. It is equal to the number of radians covered in 1 sec.


→ The unit of angular frequency is radian/sec.

$$\omega = 2\pi f$$

$$\therefore f = \frac{1}{T}$$

$$\omega = \frac{2\pi}{T}$$

Spiral

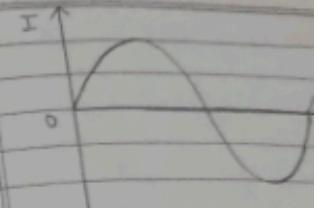

7. Phase : It is denoted by ϕ . It is the phase angle at any instant.


values of AC quantities

1. Peak value
2. Average value
3. RMS (root mean square) value

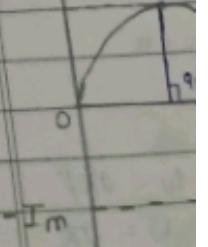
1. Peak value :-
maximum value. This value is denoted by I_m .

The peak value

maximum value. This value is denoted by I_m .



Date.....

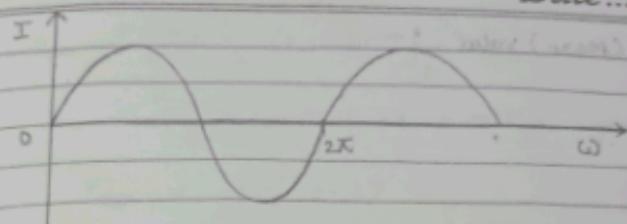

2. Phase : It is denoted as ' ϕ '.
It is the fraction of the time period or cycle known as phase.


$$\phi = 2\pi$$

Values of AC quantities -

There are three types of values in A.C. circuit -


1. Peak value
2. Average value
3. RMS (root mean square) Effective value

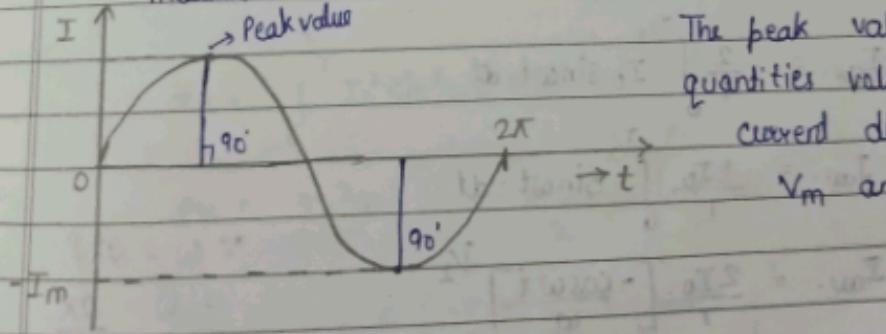1. Peak value :- The maximum value attained by the alternate quantity during one cycle is c/a as peak value. This is also c/a maximum value of AC quantities. The peak value in sinusoidal alternating quantity obtains its maximum value at 90° .



The peak value of alternating quantities voltage and current denoted by V_m and I_m

2. Average (Mean) value :-

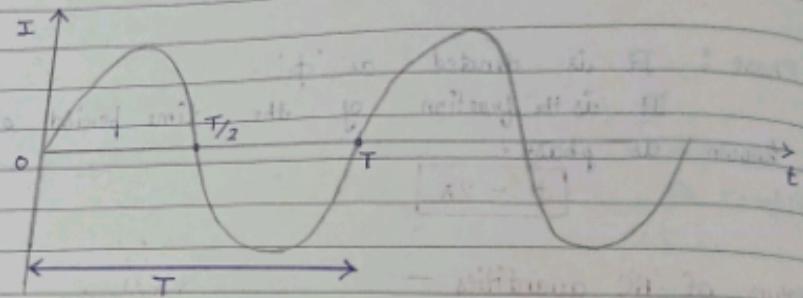

$$I = I_0 \sin \omega t$$

$I_{av.} = \frac{\text{Area under half cycle}}{\text{length of half cycle}}$

$$I_{av.} = \frac{\int_0^{T/2} I dt}{T/2}$$

$$I_{av.} = \frac{\int_0^{T/2} I_0 \sin \omega t dt}{T/2}$$

$$I_{av.} = \frac{2}{T} \int_0^{T/2} I_0 \sin \omega t dt$$

$$I_{av.} = \frac{2 I_0}{T} \int_0^{T/2} \sin \omega t dt$$

$$I_{av.} = \frac{2 I_0}{T} \left[-\frac{\cos \omega t}{\omega} \right]_0^{T/2}$$

$$\because \omega = 2\pi f \\ \Rightarrow \omega = \frac{2\pi}{T}$$

Spiral

R → Heat dissipation
 M → Energy stored in magnetic form

C → Energy stored in electric form

Date.....

$$I_{av} = -\frac{2I_0}{T} \left[\frac{1}{\omega} (\cos \omega t) \right]_0^T$$


$$I_{av} = -\frac{2I_0}{2\pi} \left[\frac{\cos 2\pi \times T}{T} - \cos 0 \right]$$

$$I_{av} = -\frac{I_0}{\pi} [-1 - 1]$$

* $I_{av} = \frac{2I_0}{\pi} = 0.637 I_0$

* $I_{av} = 63.7\% \text{ of } I_0$

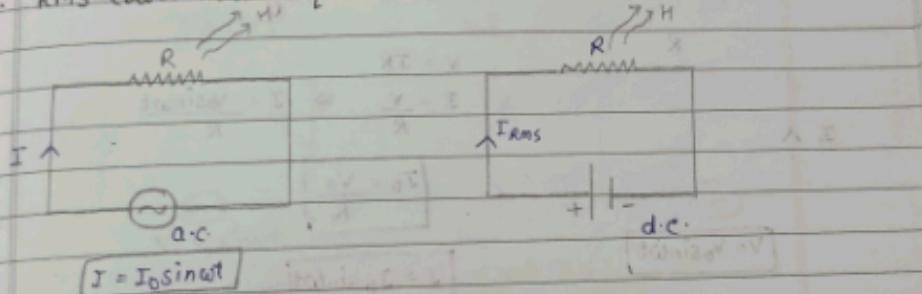Ques. RMS (Root mean square or effective value) :-



$$I = I_0 \sin \omega t$$

$$H = I^2 RT \Rightarrow H = I_{0\text{rms}}^2 RT \quad \text{for d.c. S.K.T.}$$

$$H = I_0^2 \sin^2 \omega t \times R \times T$$

$$\int dH = \int_0^T I^2 R dt$$

$$H = \int_0^T I_0^2 \sin^2 \omega t R dt$$

$$H = I_0^2 R \int_0^T \left(1 - \frac{\cos 2\omega t}{2} \right) dt$$

$$H = \frac{I_0^2 R}{2} \left[T - \frac{1}{2\omega} \sin 2\omega t \right]_0^T$$

Spiral

$$H = \frac{I_0^2 R}{2} \left[T - \frac{1}{2\omega} (\sin 4\omega - \sin 0) \right]$$

Date.....

$$I_{RMS} = \frac{I_0^2 R}{2} [T] \rightarrow (2)$$

by eqn (1) & (2) —


$$\frac{I_0^2 R}{2} T = I_{RMS}^2 \times R \times T$$

$$\frac{I_0^2}{2} = I_{RMS}^2$$


$$I_{RMS} = \frac{I_0}{\sqrt{2}}$$

$$I_{RMS} = 0.707 I_0$$

Phasor diagram

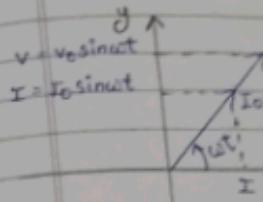

#. AC circuit with resistance only

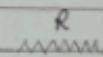

$$V = IR$$


$$I = \frac{V}{R} \Rightarrow I = \frac{V_0 \sin \omega t}{R}$$

$$I_0 = \frac{V_0}{R}$$

$$V = V_0 \sin \omega t$$

$$I = I_0 \sin \omega t$$


*. Wave form presentation :-

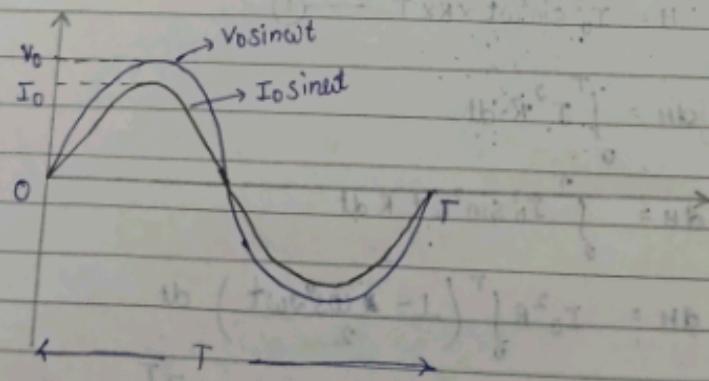

Date, 2019

Nikita


Phasor diagram —

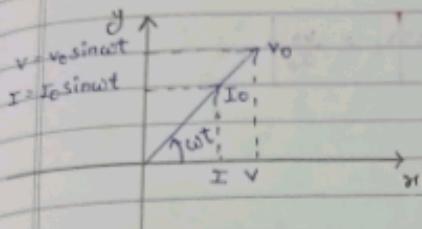

$$\phi = 0^\circ$$

$$I \propto V$$

A.C circuit with inductor only :-

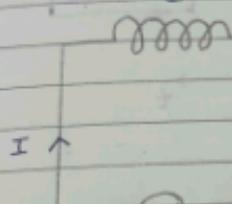

$$e = -L \frac{dI}{dt}$$

$$V = -e$$

$$V = -[-L \frac{dI}{dt}]$$

$$V = L \frac{dI}{dt}$$

$$dI = \frac{V}{L} dt \Rightarrow dI = \frac{V_0 \sin \omega t}{L} dt$$

$$\int dI = \int \frac{V_0 \sin \omega t}{L} dt \Rightarrow I = \frac{V_0}{L} \int \sin \omega t dt$$

$$I = \frac{V_0}{L} \left[-\frac{\cos \omega t}{\omega} \right] \Rightarrow I = \frac{-V_0}{\omega L} \cos \omega t$$

$$I = \frac{-V_0}{\omega L} (\sin(\frac{\pi}{2} - \omega t)) \Rightarrow I = \frac{V_0 \sin(\omega t - \frac{\pi}{2})}{\omega L}$$

$$I = \frac{V_0}{\omega L} \sin(\omega t - \frac{\pi}{2})$$

Spiral

Date.....


$$\frac{V_0}{\omega L} = I_0$$

$$\omega L = \frac{V_0}{I_0}$$

$$[\omega L = X_L]$$

$$X_L = \frac{V_0}{I_0}$$

Wave form diagram —

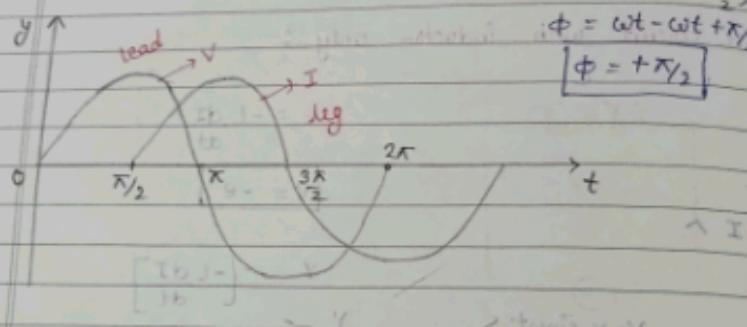


$$\phi = wt - (wt - \frac{\pi}{2})$$

$$\phi = wt - wt + \frac{\pi}{2}$$

$$[\phi = +\frac{\pi}{2}]$$

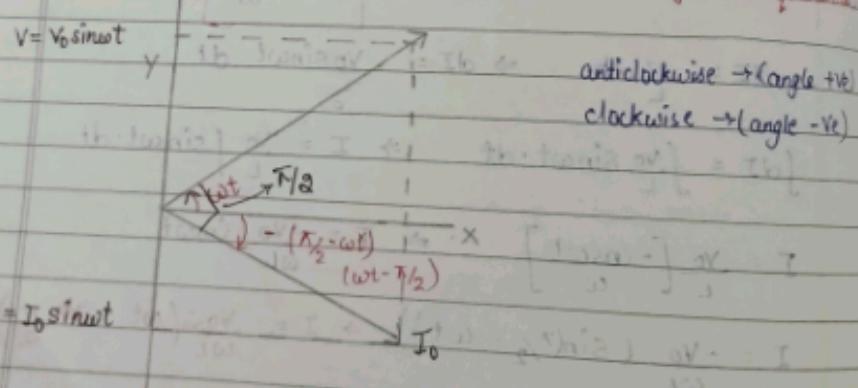Phasor diagram (Vector representation of two quantities)



$$I = I_0 \sin \omega t$$

$V = V_0 \sin \omega t$


anticlockwise \rightarrow (angle +ve)

clockwise \rightarrow (angle -ve)

④ Wave form

Date.....

AC circuit with capacitor only :-

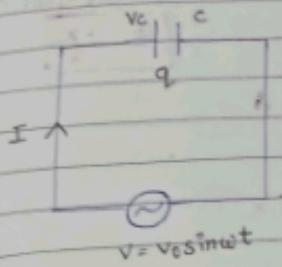

V_C = across the capacitor voltage

$$V_C = V$$

$$\frac{q}{C} = V_0 \sin \omega t$$

$$q = CV_0 \sin \omega t$$

$$I = \frac{dq}{dt}$$

$$I = \frac{d}{dt} (CV_0 \sin \omega t)$$

$$I = CV_0 \omega \cos \omega t$$

$$I = CV_0 \omega \sin\left(\frac{\pi}{2} + \omega t\right)$$


max. value of current $\leq I_0 = CV_0 \omega$

$$\frac{V_0}{I_0} = \frac{1}{C\omega} \Rightarrow X_C = \frac{1}{\omega C}$$

X_C = capacitive reactance

$$I = I_0 \sin(\omega t + \frac{\pi}{2})$$


① Wave form diagram

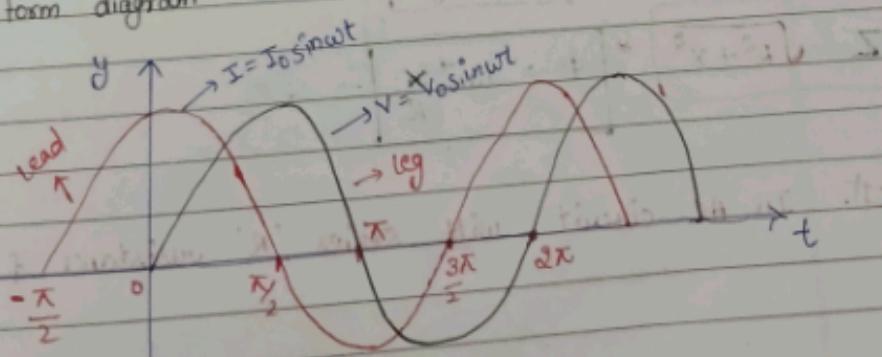

$$Z = \frac{V}{I}$$


Date.....

Phasor diagram -

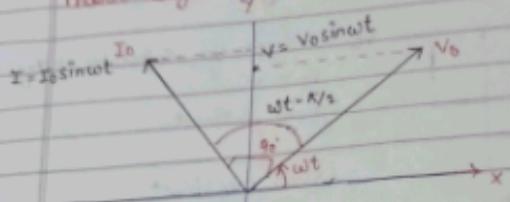

Phase difference -

$$\phi = \omega t - (\omega t + \pi/2)$$

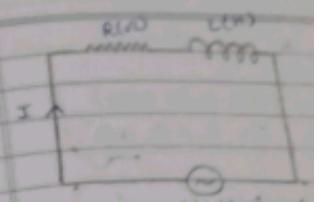

Complex Impedance :-


For an AC circuit the ratio of voltage phasor and the current phasor is known as complex quantity and is known as ~~clock~~ complex Impedance. It is represented by 'Z'. Its real part is c/a resistance and its imaginary part is c/a reactance.

Complex Impedance (Z) = Resistance + j (Reactance)

$$Z = R + jX$$

$$Z = \sqrt{R^2 + X^2} \quad \phi = \tan^{-1} \frac{X}{R}$$

wave form diagram -

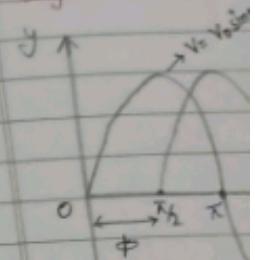


Phasor diagram →

In AC circuit, with series 'R' resistance & 'L' (inductor)

Spiral

phase difference -
 $\omega t - (\omega t + \frac{\pi}{2})$
 $= -\frac{\pi}{2}$

Date.....

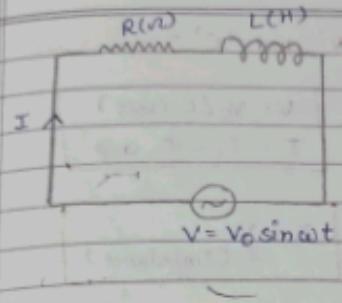

$$V = (V_0 L \omega) \text{ Volt}$$

$$I = I_0 L \omega \quad Z = R$$

$$Z = \frac{V}{I} \rightarrow Z = \text{Impedance}$$

$$Z = R + jX_L$$

$$Z = \sqrt{R^2 + X_L^2}$$


$$X_L = \omega L$$

$$X_L = 2\pi f L$$


$$\phi = \tan^{-1}\left(\frac{X_L}{R}\right)$$

ratio of
is known as
complex Impedance.
1 part is
is c/a

wave form diagram -

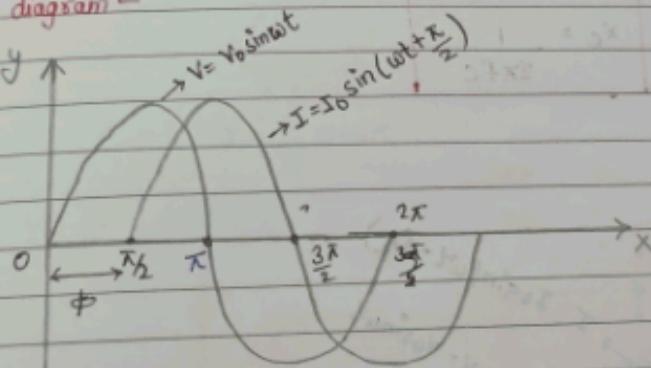


Phase diagram →

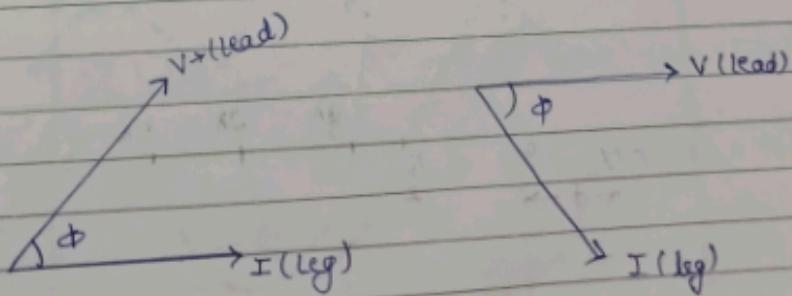

L' (inductor):-

Date.....

Q. AC circuit with series 'R' and 'C'

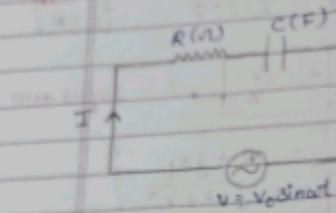

$$V = V_0 \angle 0^\circ \text{ volt}$$

$$I = I_0 \angle \phi \text{ amp.}$$

$$I = \frac{V}{Z} \quad (\text{Impedance})$$

$$Z = R - jX_C$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$j\omega = jX_C$$

$$j\omega C = jX_C$$


$$X_C = \frac{1}{\omega C}$$

$$X_C = \frac{1}{2\pi f C}$$

① Phase diagram

Q. AC circuit


Wave form diagram -

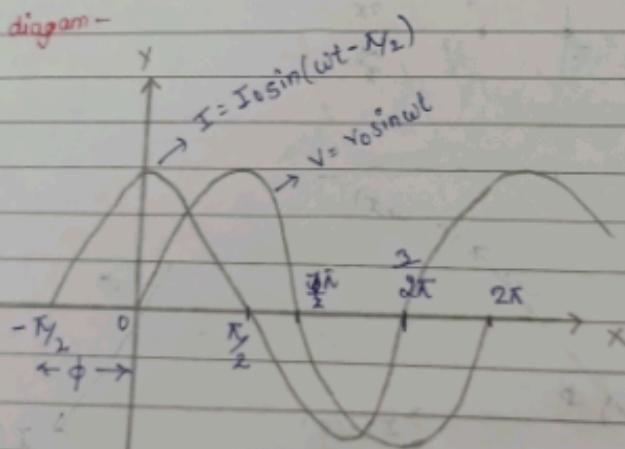


Social

Date.....

Q. Phasor diagram -

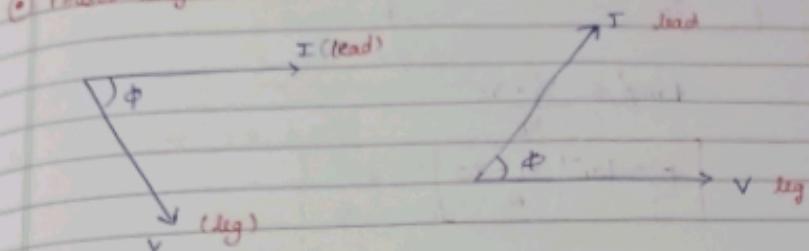


Q. AC circuit with Series in RLC

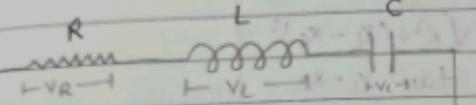

$$I = I_0 \sin \omega t$$

$$\text{Let } V_L > V_C \\ X_L > X_C$$

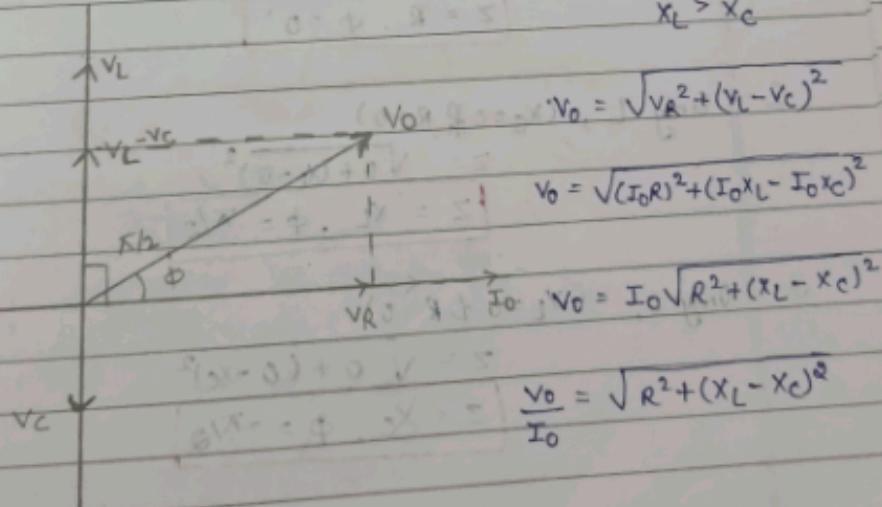

Spiral

Date.....

$$Z = \frac{V_0}{I_0} = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\tan\phi = \frac{V_L - V_C}{V_R}$$

$$\phi = \tan^{-1} \frac{X_L - X_C}{R}$$

$$V = V_0 \sin(\omega t + \phi)$$

Summary :

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\phi = \tan^{-1} \frac{X_L - X_C}{R}$$

1. Only R ($X_L = 0, X_C = 0$)

$$Z = \sqrt{R^2 + (0-0)^2}$$

$$Z = \sqrt{R^2}$$

$$Z = R, \phi = 0^\circ$$

2. Only L ($X_C = 0 \neq R = 0$)

$$Z = \sqrt{0 + (X_L - 0)^2}$$

$$Z = X_L, \phi = \pi/2$$

3. Only C ($X_L = 0 \neq R = 0$)

$$Z = \sqrt{0 + (0 - X_C)^2}$$

$$Z = X_C, \phi = -\pi/2$$

Serial

Date.....

4 R-L CKT ($X_C = 0$)

$$Z = \sqrt{R^2 + X_L^2}$$

$$\phi = \tan^{-1}\left(\frac{X_L}{R}\right)$$

5 R-C CKT ($X_L = 0$)

$$Z = \sqrt{R^2 + X_C^2}$$

$$\phi = -\tan^{-1}\left(\frac{X_C}{R}\right)$$


6 Only L-C CKT ($R=0$)

$$Z = |X_L - X_C|$$

$$\phi = \pm \pi/2$$

and from factors

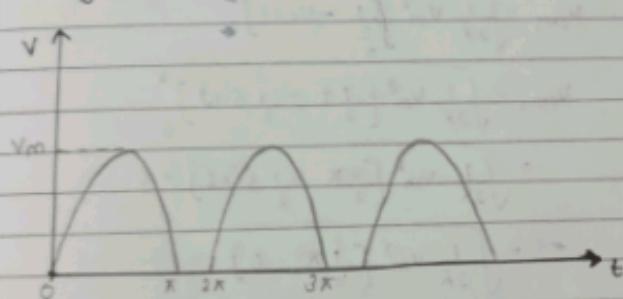Ques. Find the average value, RMS value \uparrow of the voltage shown in fig.



$V_{AV.} = \text{area under 1 cycle}$
time period

$$\int_0^{2\pi} V(t) dt = \int_0^\pi V_m \sin t dt$$

$$= V_m \int_0^\pi \frac{\sin t \cdot dt}{2\pi}$$

$$= V_m \underbrace{\left[-\cos t \right]_0^\pi}_{2\pi}$$

Spiral

Date.....

$$-\frac{V_m}{2\pi} [\cos \pi - \cos 0]$$

$$-\frac{V_m}{2\pi} [-1 - 1] = \frac{2V_m}{2\pi} = \frac{V_m}{\pi}$$

$$V_{avg} = \frac{V_m}{\pi} \quad \text{Ans.}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V_m^2 \sin^2 t dt}$$

$$V_{rms} = \sqrt{\frac{1}{T} V_m^2 \int_0^{\pi} \sin^2 t dt}$$

$$= \sqrt{\frac{1}{T} \frac{V_m^2}{2} \left[1 - \cos t \right]_0^{\pi}}$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} V_m^2 \left[\frac{1}{2} - \frac{1}{2} \cos \pi \right]}$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} V_m^2 \left[\frac{1}{2} + \frac{1}{2} \sin 0 \right]}$$

$$= \sqrt{\frac{1}{2\pi} V_m^2 \left[\frac{1}{2}\pi - \frac{1}{2} \sin 0 \right]} = 0$$

$$= \sqrt{\frac{1}{2\pi} V_m^2 \left[\frac{1}{2}\pi - 0 \right]}$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} V_m^2 \times \frac{1}{2}\pi}$$


$$V_{rms} = \frac{V_m \times \sqrt{\frac{\pi}{2}}}{\sqrt{2\pi}}$$

$$V_{rms} = \frac{V_m}{2} \quad \text{Ans.}$$

Form factor

Peak factor = $\frac{V_m}{V_{rms}}$

Ques-2 Find the aver factor of V_m

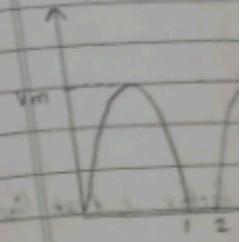


Date.....

Form factor = $\frac{V_{rms}}{V_{av.}} = \frac{V_m/\sqrt{2}}{V_m/\pi} = \frac{\pi}{2}$

Ans.

Peak factor = $\frac{V_m}{V_{rms}} = \frac{2V_{rms}}{V_{rms}} = 2$

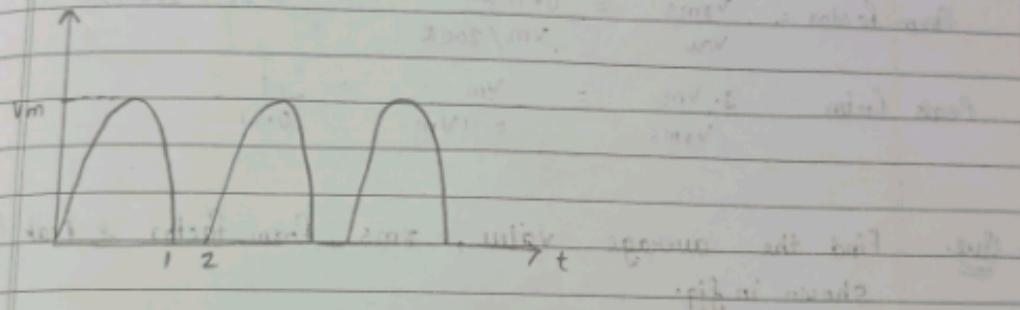Ques. Find the average value, rms value, form factor & Peak factor of voltage shown in fig.



$$= \int_0^T V_m \sin t \cdot dt$$

$$V_m \int_0^T \sin t \cdot dt$$

$$= -\frac{V_m}{2\pi} [\cos t]_0^T$$

$$= -\frac{V_m}{2\pi} [1 - \cos 0]$$

$$V_{av.} = -\frac{V_m}{2\pi} [\cos 1 - 1] = -\frac{V_m}{2\pi} [0.99 - 1] = \frac{V_m}{200\pi}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V_m^2 \sin^2 t \cdot dt} \Rightarrow V_{rms} = \sqrt{\frac{1}{T} V_m^2 \left[\frac{1}{2} t - \frac{1}{4} \cos 2t \right]_0^T}$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} V_m^2 \left[\frac{1}{2} - \frac{1}{4} \cos 2\pi \right] - \left(0 - \frac{1}{4} \right)}$$

$\cos\theta = 0.997$
 $\sin\theta = 0.034$ Date.


$$\begin{aligned}V_{rms} &= \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{2}(1 - \cos\theta)} \\&= \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{2}(1 - 1 \times 0.034)} \\&= \frac{V_m}{\sqrt{2}} \sqrt{1 \times 0.9830}\end{aligned}$$

$V_{rms} = 0.11 V_m$

$$\text{Form factor} = \frac{V_{rms}}{V_{av}} = \frac{0.11 V_m}{3400/200\pi} = 0.11 \times 200\pi$$

$$\text{Peak factor} = \frac{I_{av}}{V_{rms}} = \frac{V_m}{0.11 V_m} = \frac{1}{0.11}$$

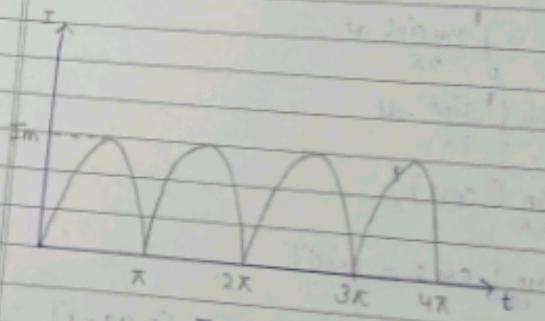Ques. Find the average value, I_{rms} , form factor & peak factor shown in fig.



$$I = I_0 \sin \omega t$$

$$I_{av} = \int_0^T I dt$$

$$I_{av} = \frac{1}{T} \int_0^T I_0 \sin \omega t dt$$

Spiral

Date.....

$$I_{av} = -\frac{I_0}{\pi} [\cos t]_0^\pi \\ = -\frac{I_0}{\pi} [\cos \pi - \cos 0] \\ = -\frac{I_0}{\pi} (-1 - 1)$$

$$I_{av} = \frac{2 I_m}{\pi}$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \sin^2 t dt} \\ = \sqrt{\frac{1}{\pi} I_m^2 \int_0^{\pi} \left[\frac{1}{2} - \frac{1}{4} \sin 2t \right]} \\ = \sqrt{\frac{1}{\pi} I_m^2 \left[\frac{1}{2}t - \frac{1}{4} \sin 2t \right]_0^\pi} \\ = \sqrt{\frac{1}{\pi} I_m^2 \left[\frac{1}{2}\pi - \frac{1}{4} \sin 2\pi \right]} = 0 \\ = \sqrt{\frac{1}{\pi} I_m^2 \frac{1}{2}\pi}$$


$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$\text{form factor} = \frac{I_{rms}}{I_{av.}} = \frac{I_m/\sqrt{2}}{2 I_m/\pi} = \frac{\pi}{2\sqrt{2}}$$

$$\text{Peak factor} = \frac{I_m \times \sqrt{2}}{I_m} = \sqrt{2}$$

Date.....

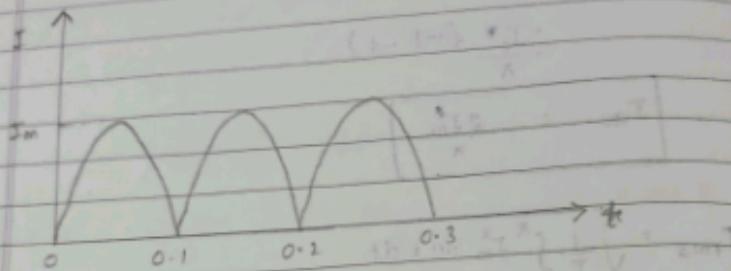Ques. Find the average value, rms value, form & Peak factor of the current shown in fig.



$$I_{av} = \frac{1}{T} \int_0^{T/2} I_m \sin \omega t \cdot dt$$

$$= \frac{-I_m}{\omega} [\cos \omega t] \Big|_0^{T/2}$$

$$I_{av} = -\frac{I_m}{\omega} [\cos \omega t - \cos 0]$$

$$I_{av} = -\frac{I_m}{\omega} [0.99 - 1] = -\frac{I_m}{\omega} \times [-0.01] = \frac{I_m}{20}$$

$$\cos \omega t = 1 - \frac{1}{20} \sin^2 \omega t$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^{T/2} I_m^2 \sin^2 \omega t \cdot dt}$$

$$= \sqrt{\frac{1}{T} I_m^2 \int_0^{T/2} \frac{1}{2} (1 - \cos 2\omega t) \cdot dt}$$

$$I_m \sqrt{\frac{1}{T} \int_0^{T/2} \left[\frac{1}{2} + \frac{1}{4} \sin 2\omega t \right] dt}$$

$$\frac{I_m}{\sqrt{0.1}} \sqrt{\left[\frac{1}{2} \times 0.1 - \frac{1}{4} \sin 2 \times 0.1 \right]} = 0$$

$$I_{rms} = \frac{I_m}{\sqrt{0.1}} \sqrt{\frac{1}{20} - \frac{1}{4}}$$


$$= \frac{I_m}{\sqrt{0.1}} \sqrt{\frac{1}{20} - \frac{1}{4}}$$

$$= \frac{I_m}{\sqrt{0.1}} \sqrt{1 - \frac{2}{20}}$$

$$= \frac{I_m}{\sqrt{0.1}} \sqrt{\frac{5}{20}}$$

$$I_{rms} =$$

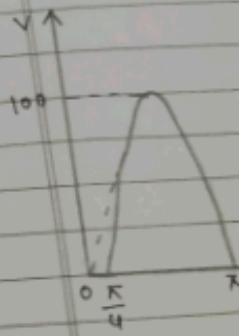Ques. Find the average value shown in wave



V_{av}

V_{avg}

Spiral

Peak factor

Date.....

$$I_{rms} = \frac{Im}{\sqrt{0.1}} \sqrt{\frac{1}{20} - \frac{1}{4} \sin 0.2}$$

$$I_{rms} = \frac{Im}{\sqrt{0.1}} \sqrt{\frac{1}{20} - \frac{1}{4} \times 0.19} = \frac{Im}{\sqrt{0.1}} \sqrt{\frac{1 - 0.19}{20}}$$

$$= \frac{Im}{\sqrt{0.1}} \sqrt{\frac{1 - 0.19 \times 5}{20}} = \frac{Im}{\sqrt{0.1}} \sqrt{\frac{1 - 0.95}{20}} = \frac{Im}{\sqrt{0.1}} \sqrt{\frac{0.05}{20}}$$


$$= \frac{Im}{\sqrt{0.1}} \sqrt{\frac{5}{2000}} = \frac{Im}{\sqrt{0.1}} \sqrt{\frac{1}{400}} = \frac{Im}{\sqrt{0.1} \times 20}$$

$$I_{rms} = \frac{Im}{\sqrt{0.1} \times \sqrt{0.1}} = I_{rms} = \frac{Im}{20 \times 0.31}$$

$$\boxed{I_{rms} = \frac{Im}{6.2}}$$

Ques. Find the average and effective value of the sinusoidal shown in wave form.

V_{av} = 37.17 V

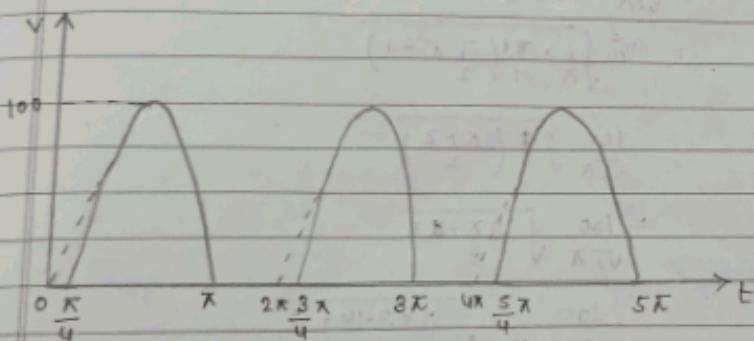

$$V_{av} = \int_{\pi/4}^{\pi} V_0 \sin t dt$$

$$= \frac{-V_0}{2\pi} [\cos t]_{\pi/4}^{\pi} = \frac{-V_0}{2\pi} [\cos \pi - \cos \frac{\pi}{4}]$$

$$V_{av} = \frac{-V_0}{2\pi} \left[-1 - \frac{\sqrt{3}}{2} \right] = \frac{-V_0}{2\pi} \left(-1 - \frac{1}{\sqrt{2}} \right)$$

$$= \frac{-50}{\pi} \left[\frac{-\sqrt{2} - 1}{\sqrt{2}} \right] = \frac{50}{\pi \sqrt{2}} [1 + \sqrt{2}]$$

$$\boxed{V_{av} = 37.17 V}$$

Spiral

$$\begin{aligned}
 V_{rms} &= \sqrt{\frac{1}{T} V_m^2 \sin^2 t \cdot dt} \\
 &= \sqrt{\frac{1}{2\pi} V_m^2 \int_{\pi/4}^{\pi/2} 1 - \cos \omega t \cdot dt} \\
 &= \sqrt{\frac{1}{2\pi} V_m^2 \left[\frac{1}{2}t - \frac{\sin \omega t}{\omega} \right]_{\pi/4}^{\pi/2}} \\
 &= \sqrt{\frac{1}{2\pi} V_m^2 \left[\frac{1}{2}\pi - \frac{\sin \pi}{4} \right] - \left[\frac{1}{2} \times \frac{\pi}{4} - \frac{\sin \pi/2}{4} \right]} \\
 &= \sqrt{\frac{1}{2\pi} V_m^2 \left[\frac{1}{2}\pi - 0 \right] - \left[\frac{\pi}{8} - \frac{1}{4} \right]} \\
 &= \sqrt{\frac{1}{2\pi} V_m^2 \left[\frac{1}{2}\pi - \frac{\pi}{8} + \frac{1}{4} \right]} \\
 &= \sqrt{\frac{1}{2\pi} V_m^2 \left[\frac{3\pi}{8} + \frac{1}{4} \right]} \\
 &= V_m \sqrt{\frac{1 \times 3.1}{4} \left(\frac{3\pi}{2} + 1 \right)} \\
 &= \frac{100}{\sqrt{2\pi}} \sqrt{\frac{3}{4} \left(\frac{3\pi+2}{2} \right)} \\
 &= \frac{100}{\sqrt{2\pi}} \sqrt{\frac{3\pi+2}{8}}
 \end{aligned}$$

$$= \frac{100}{\sqrt{2} \times 3.14} \sqrt{\frac{3 \times 3.14 + 2}{8}}$$


$$= \frac{100}{4 \times 4.44} \sqrt{\frac{9.42 + 2}{8}}$$

$$= 22.52 \sqrt{\frac{11.42}{8}} = 22.52 \times \sqrt{1.4275}$$

$$V_{rms} = 24.75$$

Ques

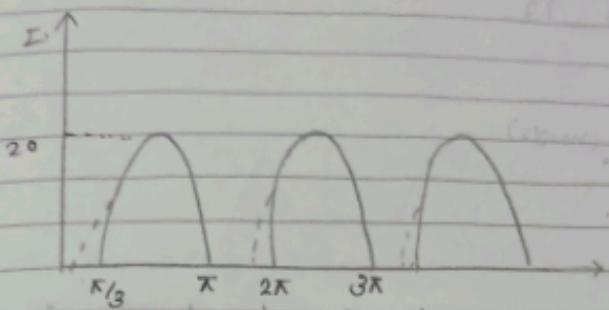Find the average and effective value of the sinusoidal waveform shown in fig.



$$I = \int_{\pi/3}^{\pi} \frac{I_m \sin t}{2\pi} dt = \frac{I_m}{2\pi} \int_{\pi/3}^{\pi} \sin t \cdot dt = -\frac{I_m}{2\pi} [\cos t]_{\pi/3}^{\pi}$$

$$= -\frac{I_m}{2\pi} [\cos \pi - \cos \frac{\pi}{3}] = -\frac{I_m}{2\pi} [-1 - \frac{1}{2}]$$

$$= -\frac{I_m}{2\pi} \left[-\frac{3}{2} \right] = \frac{I_m}{2\pi} \left[\frac{3}{2} \right]$$

$$= \frac{I_m}{2\pi} \left[\frac{1 + \sqrt{2}}{\sqrt{2}} \right] = \frac{I_m}{2\pi} \left[\frac{1 + \sqrt{2}}{\sqrt{2}} \right]$$

$$I_{av.} = \frac{I_m}{2\pi} \cdot \left(\frac{1 + \sqrt{2}}{\sqrt{2}} \right)$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_{\pi/3}^{\pi} I_m^2 \sin^2 t \cdot dt} = \sqrt{\frac{1}{2\pi} I_m^2 \int_{\pi/3}^{\pi} \frac{1 - \cos 2t}{2} \cdot dt}$$


$$= \sqrt{\frac{1}{2\pi} I_m^2 \left[\frac{1}{2} t - \frac{1}{4} \sin 2t \right]_{\pi/3}^{\pi}}$$

$$= \sqrt{\frac{1}{2\pi} I_m^2 \left[\left(\frac{\pi}{2} - \sin \frac{\pi}{2} \right) - \left(\frac{\pi}{6} - \sin \frac{\pi}{6} \right) \right]} = \sqrt{\frac{1}{2\pi} I_m^2 \left(\frac{\pi}{2} - 1 \right) - \left(\frac{\pi}{6} - \frac{1}{2} \right)}$$

$$\sqrt{\frac{1}{2\pi} I_m^2 \left(\frac{\pi}{2} - 1 - \frac{\pi}{6} + \frac{1}{2} \right)} = \sqrt{\frac{1}{2\pi} I_m^2 \left(\frac{\pi}{3} - \frac{1}{2} \right)} = I_{rms}$$

Spiral

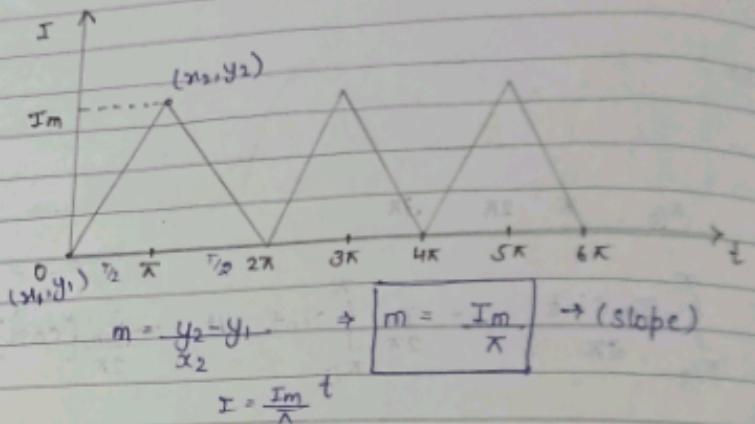B. Determine the average value, rms value and h.m.b. for current wave form shown in fig.



$I_{av.} = \frac{\text{Area under 1 cycle}}{\text{half period}}$

$$I_{av.} = \int_0^{\frac{\pi}{2}} \frac{Im \cdot t}{\pi} dt$$

$$I_{av.} = \frac{Im}{\pi^2} \left[\frac{t^2}{2} \right]_0^{\frac{\pi}{2}}$$

$$\therefore I_{av.} = \frac{Im}{\pi^2} \left[\frac{\pi^2}{2} \right]$$

$$I_{av.} = \frac{Im}{2}$$

$$I_{rms} = \sqrt{\frac{1}{T} \int \frac{Im^2}{\pi^2} t^2 dt}$$

$$= \sqrt{\frac{1}{\pi^3} Im^2 \left[\frac{t^3}{3} \right]_0^{\frac{\pi}{2}}}$$

$$= \sqrt{\frac{1}{3\pi^3} Im^2 \left[\frac{\pi^3}{3} \right]}$$


Date

$$I_{rms} = \frac{I_m}{\sqrt{3}}$$

$$\text{form factor} = \frac{I_{rms}}{I_{av.}} = \frac{I_m/\sqrt{3}}{I_m/2} = \boxed{\frac{2}{\sqrt{3}}} \text{ Ans.}$$

$$\text{Peak factor} = \frac{I_m}{I_{rms}} = \frac{I_m}{I_m/\sqrt{3}} = \boxed{\sqrt{3}} \text{ Ans.}$$

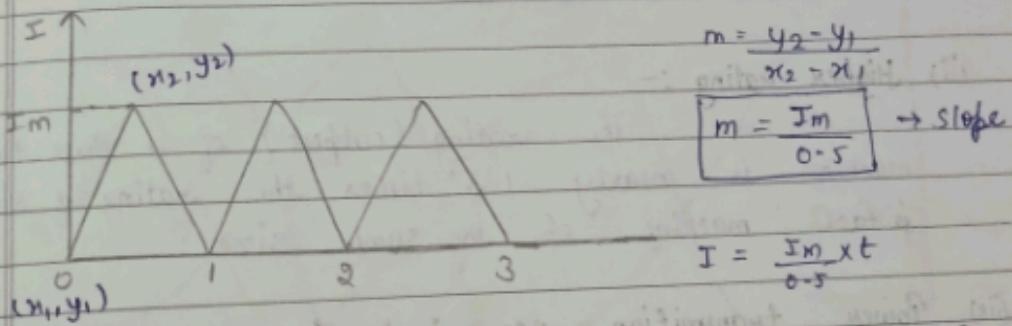Ques: Find the average value, rms value and form factor of the current wave form -



$$m = \frac{y_2 - y_1}{x_2 - x_1}$$

$$m = \frac{I_m}{0.5} \rightarrow \text{slope}$$

$$I = \frac{I_m}{0.5} \times t$$

$$I_{av.} = \frac{0.5}{0.5} \int_0^{0.5} \frac{I_m}{0.5} \cdot t \, dt \Rightarrow I_{av.} = \frac{I_m}{0.5 \times 0.5} \left[\frac{t^2}{2} \right]_0^{0.5}$$

$$I_{av.} = \frac{I_m}{0.25} \times \left[\frac{0.25 - 0}{2} \right] \Rightarrow I_{av.} = \boxed{\frac{I_m}{2}} \text{ Ans.}$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^{0.5} I_m^2 t^2 \, dt} \Rightarrow I_{rms} = \sqrt{\frac{I_m^2}{0.25 \times 0.5} \left[\frac{t^3}{3} \right]_0^{0.5}}$$

$$I_{rms} = \sqrt{\frac{I_m^2}{0.125} \left[\frac{(0.5)^3 - 0}{3} \right]} \Rightarrow I_{rms} = \sqrt{\frac{I_m^2}{0.125} \left[\frac{0.125 - 0}{3} \right]}$$

$$I_{rms} = \sqrt{\frac{I_m^2}{0.125} \times \frac{0.125}{3}} \Rightarrow \boxed{I_{rms} = \frac{I_m}{\sqrt{3}}} \text{ Ans.}$$

Spiral

Date.....

$$\text{Form factor: } \frac{I_{\text{rms}}}{I_{\text{av.}}} = \frac{I_m / \sqrt{3}}{I_m / 2} = \boxed{2/\sqrt{3}}$$

$$\text{Peak factor: } \frac{I_m}{I_{\text{rms}}} = \frac{I_m}{I_m / \sqrt{3}} = \boxed{\sqrt{3}}$$

iii Three phase AC system :-

The advantage of using three phase system over single phase system are as follows :-

(i) Constant Power : In single phase the power delivered is pulsating. The power is zero twice in each cycle. In three phase power delivered as constant when load are balanced.

(ii) Higher rating :-

The rating (output) of a three phase machine is nearly 1.5 times the rating of single phase machine of the same size.


(iii) Power transmission economical :-

Three phase transmission requires much less conductor material whereas in single phase much more require conductor materials.


(iv) Superiority of three phase induction motor : Three phase induction motor are self starting whereas single phase induction motor have no starting torque.

Date.....

Generation of three phase system:-

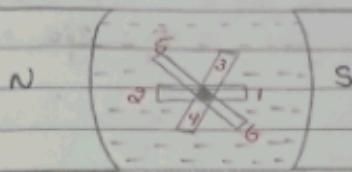

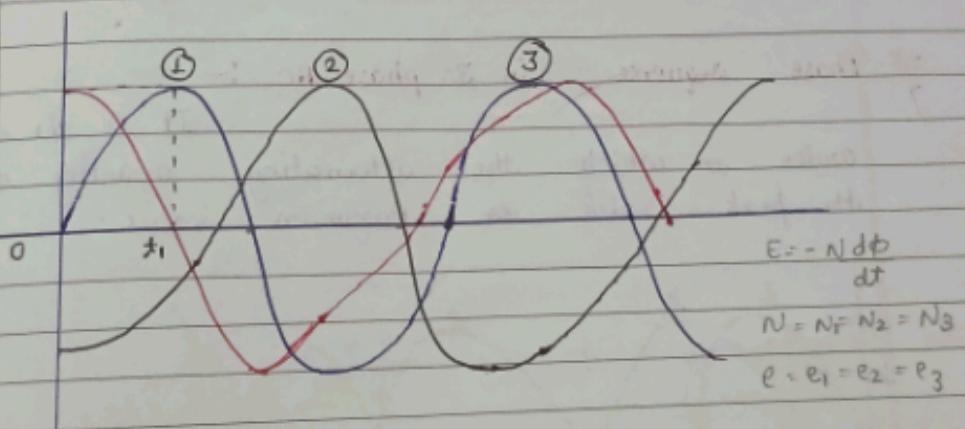Rotate these magnet anti clock wise (ωt radian).



$$e_1 = E_m \sin(\omega t) \quad \text{--- ①} \quad \text{For conductor in magnet}$$

$$e_2 = E_m \sin\left(\omega t - \frac{2\pi}{3}\right) \quad \text{--- ②}$$

$$e_3 = E_m \sin\left(\omega t - \frac{4\pi}{3}\right) \quad \text{--- ③}$$


Spiral

Date.....

$$\phi = \frac{360}{N} \text{ electrical degree}$$

$$\phi = \frac{360}{3} = 120^\circ$$


Phase diagram -

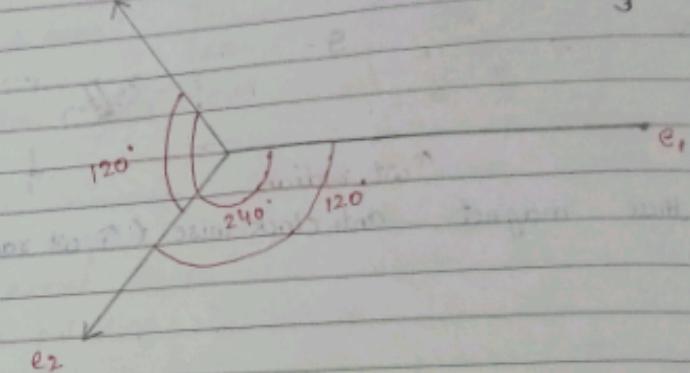

Phase sequence in 3 phase AC :-

order in which the alternating quantity attains the peak / value or maximum value.

It is the sequence

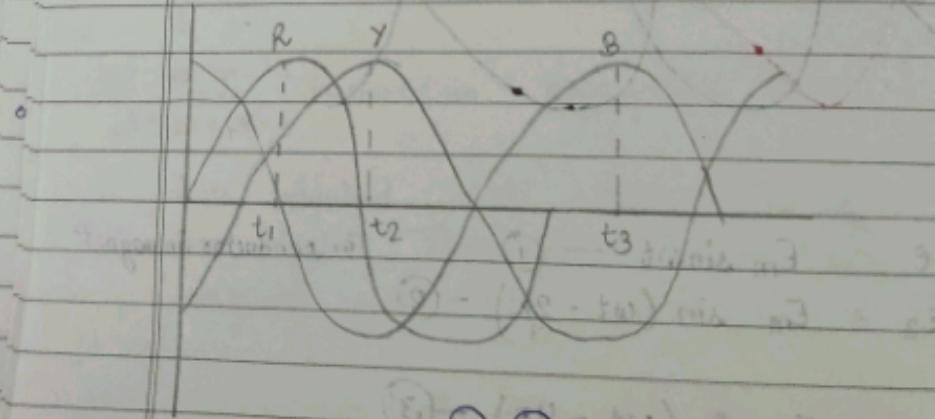

$\text{R } \text{Y } \text{B}$ = +ve phase sequence

$\text{B } \text{Y } \text{R}$ = -ve phase sequence

Date.....


* Types of 3 phase A.C.

There are two types of three phase A.C.

1. Symmetrical/balanced
2. Unsymmetrical three phase A.C.

1.

$$e = -N \frac{d\phi}{dt}$$

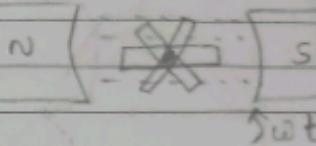


$$= N = N_1 = N_2 = N_3$$

$$= e = e_1 = e_2 = e_3$$

$$\frac{d\phi}{dt} = \frac{d\phi_1}{dt} = \frac{d\phi_2}{dt} = \frac{d\phi_3}{dt}$$

balanced / symmetrical

2. $N_1 = 200, N_2 = 300, N_3 = 500$

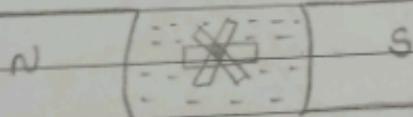

$$e = -N \frac{d\phi}{dt}$$

$$= N = N_1 \neq N_2 \neq N_3$$



$$= e = e_1 \neq e_2 \neq e_3$$

$$\frac{d\phi}{dt} = \frac{d\phi_1}{dt_1} \neq \frac{d\phi_2}{dt_2} \neq \frac{d\phi_3}{dt_3}$$

Unsymmetrical

Date.....

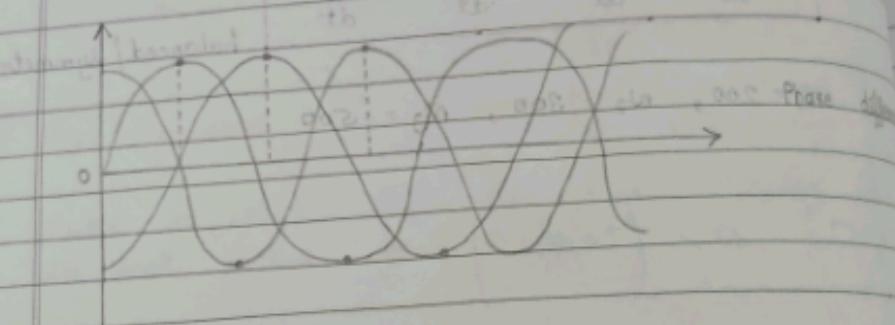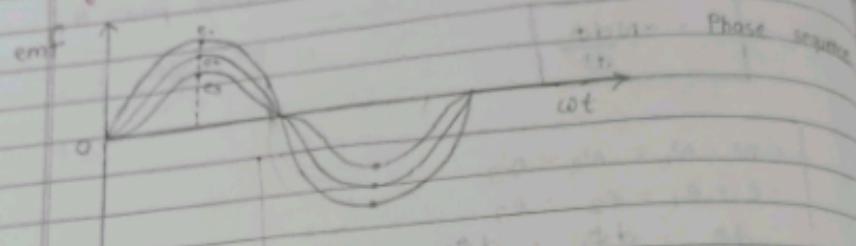Identification of phase sequence and phase difference by wave form representation




Connection of 3 phase A.C. →

- There are 2 type of connection in 3 phase A.C.
1. star connection 2. delta connection

1. Star Connection :-


where It is the type of connection
which one terminal from each binding is connect
to the common point and remaining 3 terminal
are connected to the CKT.

Spiral

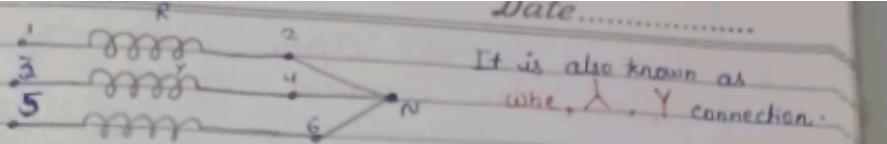

It is also known as
wye, Δ, Y connection.

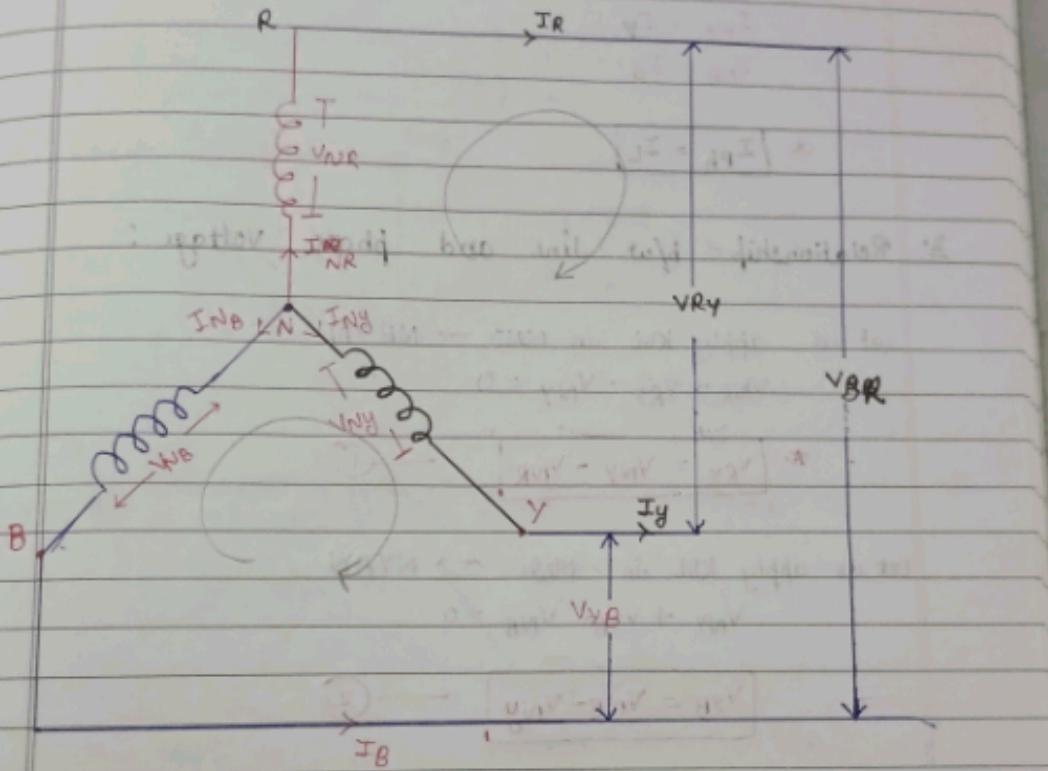- ① Standard diagram of star connection R, Y, B :-



Line quantities →

1. Line voltage $\Rightarrow V_{RY} = V_{YB} = V_{BR} = V_L$
2. Line current $\Rightarrow I_R = I_Y = I_B = I_L$

Phase quantities →

1. Phase voltage $\Rightarrow V_{NR} = V_{NY} = V_{NB} = V_{\text{Phase}}$
2. Phase current $\Rightarrow I_{NR} = I_{NY} = I_{NB} = I_{\text{Phase}}$

Spiral

Date.....

3. Relationship b/w line & phase quantities for balanced
3-phase star connected system:

4. Relationship b/w line and phase current:

$$I_{NR} = I_R$$

$$I_{NY} = I_Y$$

$$I_{NB} = I_B$$

* $I_{Ph} = I_L$

5. Relationship b/w line and phase voltage:

Let us apply KVL in Mesh \rightarrow NRYN

$$V_{NR} + V_{RY} - V_{NY} = 0$$

* $V_{RY} = V_{NY} - V_{NR}$ — (1)

Let us apply KVL in Mesh \rightarrow NYBN

$$V_{NY} + V_{YB} - V_{NB} = 0$$

$V_{YB} = V_{NB} - V_{NY}$ — (2)

Let us apply KVL in mesh \rightarrow NRBN

$$V_{NR} - V_{BR} - V_{NB} = 0$$

$V_{BR} = V_{NR} - V_{NB}$ — (3)

Date.....


from eqⁿ (1) $\rightarrow \sqrt{a^2 + b^2 + 2ab\cos\phi}$

$$V_{RY} = \sqrt{V_{NY}^2 + V_{NR}^2 + 2V_{NR}V_{NY}\cos\phi}$$

$$= \sqrt{V_{ph}^2 + V_{ph}^2 + 2V_{ph}^2\cos 60^\circ}$$

* $V_{RY} = \sqrt{3}V_{ph}$


Phasor diagram —

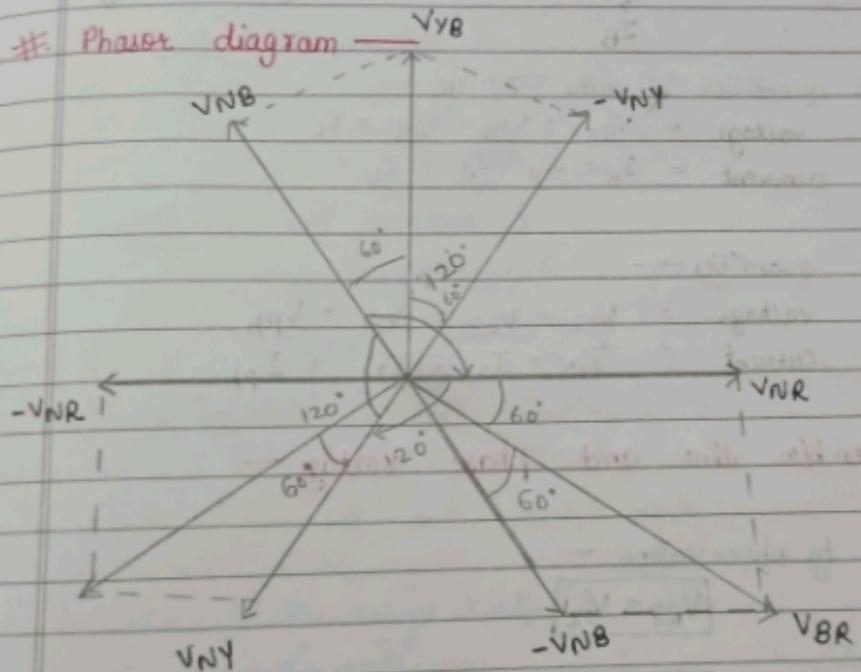

2 Delta connection :-

It is the type of connection of three phase windings where all the coils are connected back to back arrangement

Date.....

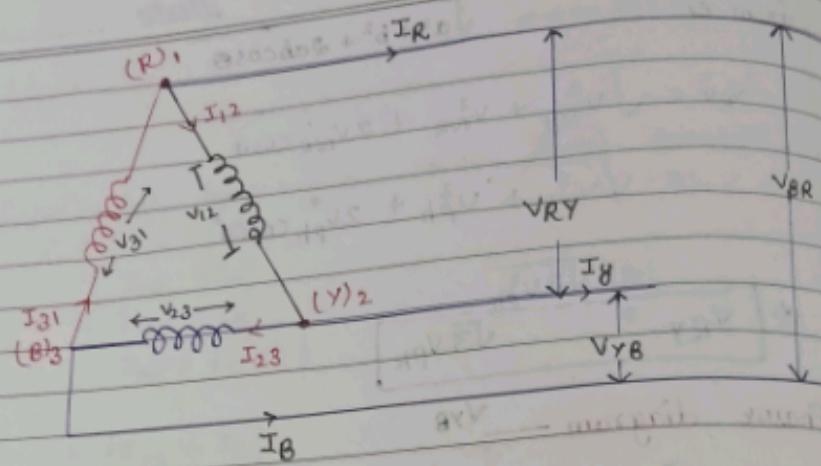

Line quantities of delta 3ϕ AC —

- Line voltage $= V_{RY} = V_{YB} = V_{BR} = V_L$
- Line current $= I_R = I_Y = I_B = I_L$

Phase quantities —

- Phase voltage $= V_{12} = V_{23} = V_{31} = V_{ph}$
- Phase current $= I_{12} = I_{23} = I_{31} = I_{ph}$

Relation b/w line and phase voltage —

Just by observation —

$$V_{RY} = V_{12}$$

$$V_{YB} = V_{23}$$

$$V_{BR} = V_{31}$$

$$V_L = V_{ph}$$

Date.....

Relation b/w line and phase current in 3φ —

$$\text{Line current} = I_R = I_y = I_B = I_L$$

$$\text{Phase current} = I_{12} = I_{23} = I_{31} = I_{ph}$$

Apply KCL at junction 1 —

$$I_{31} - I_{12} - I_R = 0$$

$$I_R = I_{31} - I_{12} \quad (1)$$

Apply KCL at junction 2 —

$$I_{12} - I_{23} - I_y = 0$$

$$I_y = I_{12} - I_{23} \quad (2)$$

Apply KCL at junction 3 —

$$I_{23} - I_{31} - I_B = 0$$

$$I_B = I_{23} - I_{31} \quad (3)$$

Taking equation (1) for resulting —


$$I_R = \sqrt{I_{31}^2 + I_{12}^2 + 2I_{31}I_{12} \cos\phi}$$

$$I_R = \sqrt{I_{ph}^2 + I_{ph}^2 + 2I_{ph} \cdot I_{ph} \cos 60^\circ}$$

$$I_R = \sqrt{I_{ph}^2 + I_{ph}^2 + I_{ph}^2}$$

$$\star \boxed{I_R = \sqrt{3} I_{ph}}$$

Phasor diagram

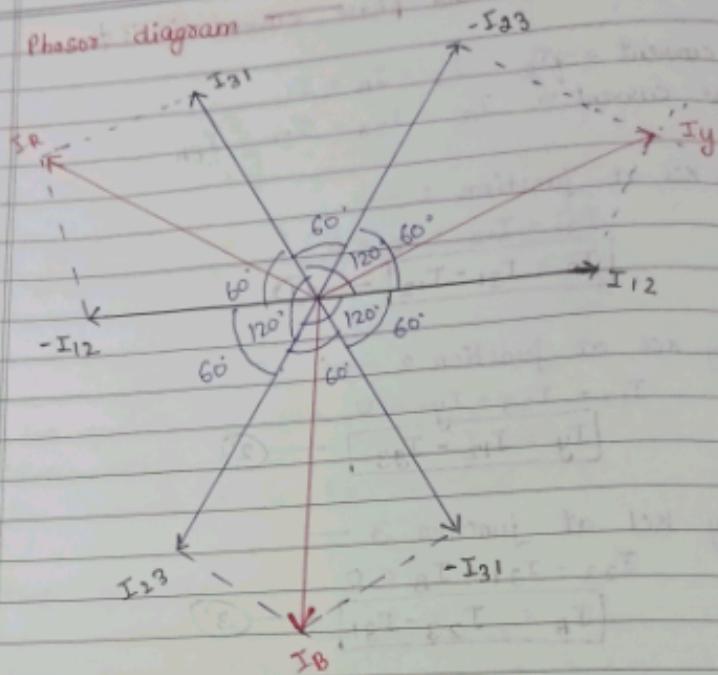

Delta

$$P_3 = V_{AB} I_{AB}$$


Power in three phase AC →

There are three types of power in single phase

1. Active Power (P) = $V_{rms} I_{rms} \cos \phi$ (watt)
2. Reactive Power (Q) = $V_{rms} I_{rms} \sin \phi$ (volt amperes)
3. Apparent Power (S) = $V_{rms} I_{rms}$ (VA) (volt amperes)

Power in three phase AC →

Star

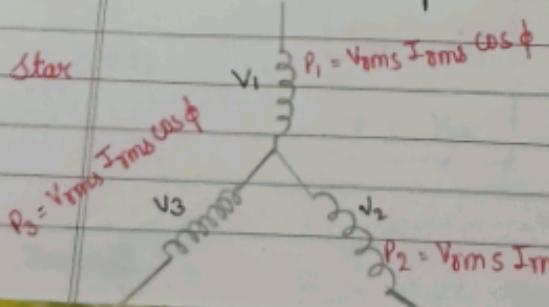

The Star Connection-

$$I_1 = I_2 = I_3 = I_{ph}$$


$$V_1 = V_2 = V_3 = V_{ph}$$

$$P_1 = P_2 = P_3 = P_T$$

$$P_{star} = 3 V_{ph} I_{ph} \cos \phi$$

Spiral

Date.....

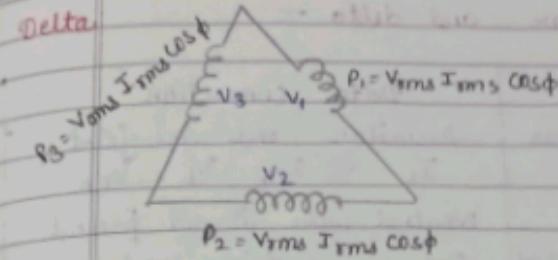

Delta connection -

$$V_1 = V_2 = V_3 = V_{ph}$$

$$I_1 = I_2 = I_3 = I_{ph}$$

$$P_1 = P_2 = P_3 = P_T$$

$$P_{\text{Delta}} = 3V_{ph} I_{ph} \cos\phi$$

Star

$$I_L = I_{ph}$$

$$V_L = \sqrt{3} V_{ph}$$

$$P_{ph} = 3 V_{ph} I_{ph} \cos\phi$$

$$P_L = \sqrt{3} V_L I_L \cos\phi$$

Delta

$$I_L = \sqrt{3} I_{ph}$$

$$V_L = V_{ph}$$

$$P_{ph} = 3 V_{ph} I_{ph} \cos\phi$$

$$P_L = \sqrt{3} V_L I_L \cos\phi$$

1. Active power in term of phase

$$P_T = 3 V_{ph} I_{ph} \cos\phi$$

Active power in term of line

$$P_L = \sqrt{3} V_L I_L \cos\phi$$

2. Reactive power in term of phase

$$Q = 3 V_{ph} I_{ph} \cos\phi$$

Reactive power in term of line

$$Q = \sqrt{3} V_L I_L \cos\phi$$

3. Apparent power in term of phase -

$$S = 3 V_{ph} I_{ph}$$

Apparent power in term of line -

$$S = \sqrt{3} V_L I_L$$

Comparison b/w star and delta -

- Star connection
 - Similar ends are joint together
 - $I_L = I_{Ph}$, $V_L = \sqrt{3} V_{Ph}$
 - Neutral wire is present
 - Both domestic and industrial load can be handled.
 - By earthing the neutral wire release and protective device can be provided by safety.

Delta connection

- Dissimilar ends are joint
- $I_L = \sqrt{3} I_{Ph}$ $V_L = V_{Ph}$
- Neutral wire is not present.
- Only industrial load can be handled.
- Due to absence of the neutral wire it is not possible.


- ** Types of measurement
- There are
 - i) Star
 - ii) Delta
 - iii) Delta
 - iv) Delta

1. Star

Measurement of three phase AC system :-

Wattmeter :-

→ measuring current
c.c. (Current coil)

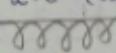

p.c. (Pressure coil) or (Potential coil)

→ measuring voltage

$$P_0 = VI \cos \phi$$

Blondel's theorem :-

According to the Blondel's theorem any 'N' phase balanced system the minimum wattmeter required for power measurement will be $(N-1)$.

Whereas for 'N' phase unbalanced system the

Spiral

Date.....

minimum number of wattmeter required will be ' N '. Here,
 $N = \text{number of phases}$


** Types of connected load in three phase (3ϕ) power measurement of balanced system :-

→ There are 4 types :-

- (i) Star connected lagging power factor load → Inductor
- (ii) Star connected leading power factor load → Capacitor
- (iii) Delta connected lagging power factor load → Inductor
- (iv) Delta connected leading power factor load → Capacitor

1. Star connected lagging power factor load :-

/2 watt power method

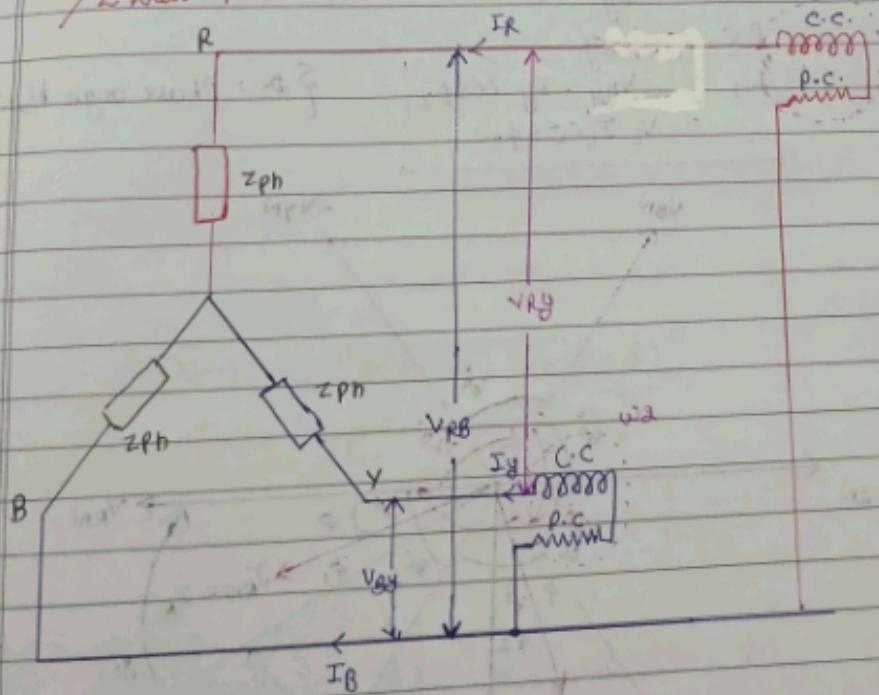

Spiral

Date.....

Since the system is balanced

$$V_L = V_{RY} = V_{YB} = V_{RB}$$

$$I_L = I_R = I_Y = I_B$$

Reading of wattmeter of ω_1

$$C.C. = I_R$$

$$P.C. = V_{RB}$$

$$\star \quad W_1 = V_{RB} I_R \cos \phi_1 \\ = V_L I_L \cos \phi_1$$

ϕ_1 = Phase angle b/w V_{Ref} & I_R


Reading of wattmeter of ω_2

$$C.C. = I_Y$$

$$P.C. = V_{BY}$$

$$\star \quad W_2 = V_{BY} I_Y \cos \phi_2 \\ = V_L I_L \cos \phi_2$$

ϕ_2 = Phase angle b/w V_{Ref} & I_Y

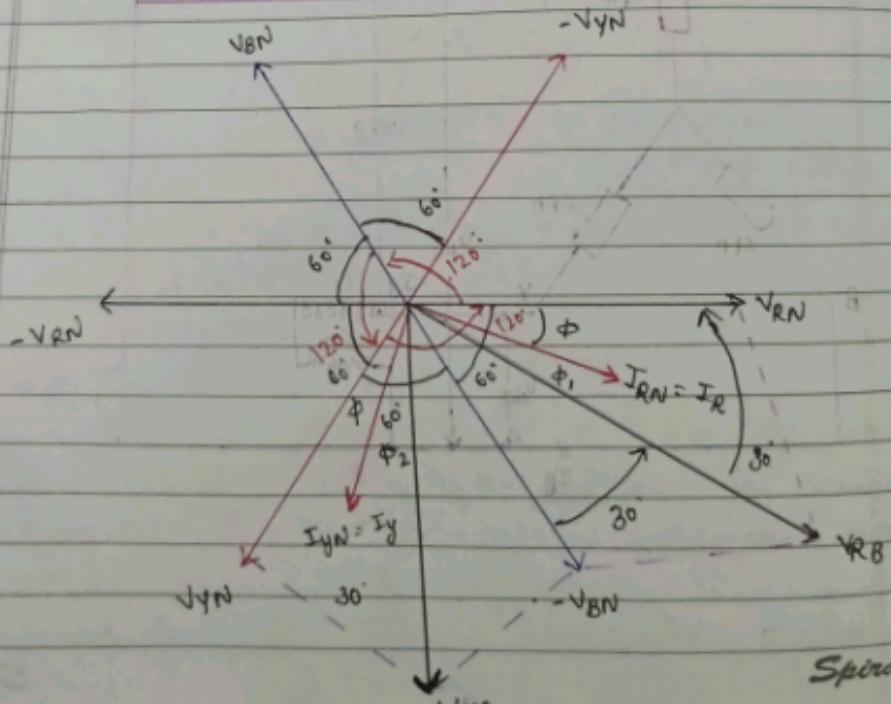

$$\phi_1 = V_{RB} + I_R$$

$$\phi_2 = V_{BY} + I_Y$$

for star connected

$$I_L = I_R = I_Y = I_B$$

$$I_{RN} = I_R$$

$$\phi_1 = 30^\circ - \phi$$

$$\phi_2 =$$

$$W_1 = V$$

$$W_2 = V$$

adding

$$W_1 + W_2 =$$

$$W_1 + W_2 =$$

$$\therefore \boxed{\cos \phi + \cos \phi}$$

$$W_1 + W_2 = V$$

$$= V$$

$$= I$$

Subtracting

$$W_2 - W_1 = V$$

$$= V$$

$$= I$$

Date.....

$$\phi_1 = V_{RB} + I_R$$

$$\phi_2 = V_{YB} + I_Y$$

for star connected balanced 3 ϕ system -

$$I_L = I_{Ph}$$

$$I_{RN} = I_R$$

$$\phi_1 = 30^\circ - \phi$$

$$\phi_2 = 30^\circ + \phi$$

$$w_1 = V_L I_L \cos(30^\circ - \phi) \quad \text{--- (1)}$$

$$w_2 = V_L I_L \cos(30^\circ + \phi) \quad \text{--- (2)}$$

adding eqn (1) and (2) —

$$w_1 + w_2 = V_L I_L \cos(30^\circ - \phi) + V_L I_L \cos(30^\circ + \phi)$$

$$w_1 + w_2 = V_L I_L [\cos(30^\circ - \phi) + \cos(30^\circ + \phi)]$$

$$\because \cos C + \cos D = 2 \cos \frac{C+D}{2} \cdot \cos \frac{C-D}{2}$$

$$w_1 + w_2 = V_L I_L \left[2 \cos \frac{(30^\circ - \phi + 30^\circ + \phi)}{2} \cdot \cos \frac{(30^\circ - \phi - 30^\circ + \phi)}{2} \right]$$

$$= V_L I_L [2 \cos 30^\circ \cdot \cos(-\phi)]$$

$$= V_L I_L \left[2 \times \frac{\sqrt{3}}{2} \cdot \cos \phi \right]$$

$$\star \boxed{w_1 + w_2 = \sqrt{3} V_L I_L \cos \phi} \quad \text{--- (3)}$$

subtracting eqn (2) - eqn (1)

$$w_2 - w_1 = V_L I_L \cos(30^\circ + \phi) - V_L I_L \cos(30^\circ - \phi)$$

$$= V_L I_L [\cos(30^\circ + \phi) - \cos(30^\circ - \phi)]$$

Date.....

$$\begin{aligned}\cos C - \cos D &= -\frac{2 \sin \frac{C+D}{2}}{2} \cdot \frac{\sin \frac{C-D}{2}}{2} \\ \omega_2 - \omega_1 &= V_L I_L \left[-\frac{2 \sin \left(30^\circ + \phi + 30^\circ - \frac{\pi}{2}\right)}{2} \cdot \frac{\sin \left(30^\circ + \phi - 30^\circ + \frac{\pi}{2}\right)}{2} \right] \\ &= V_L I_L \left[-2 \sin 30^\circ \cdot \sin \phi \right] \\ &= V_L I_L \left[-2 \times \frac{1}{2} \cdot \sin \phi \right] \\ &= -V_L I_L \sin \phi \\ \boxed{\omega_1 - \omega_2 = V_L I_L \sin \phi} \quad &\text{--- (4)}$$

Divide eqⁿ (4) / (3)

$$\begin{aligned}\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} &= \frac{V_L I_L \sin \phi}{(\sqrt{3} V_L I_L) \cos \phi} \\ \frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} &= \frac{1}{\sqrt{3}} \tan \phi\end{aligned}$$

$$\Rightarrow \boxed{\phi = \tan^{-1} \sqrt{3} \left(\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} \right)}$$

* Power factor :-

$$\boxed{\cos \phi = \cos \left[\tan^{-1} \sqrt{3} \left(\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} \right) \right]}$$